
Feedback and Flip-Flops

Philipp Koehn

7 September 2019



The Story So Far




- We can encode numbers■
- We can do calculation■
- ... but it's all a bit static■


- How about a counter?■
 - this requires "memory"

feedback

A Strange Contraption

 


Let's Turn It On

 

Electricity is on \rightarrow this opens the normally closed key

Let's Turn It On

 


Electricity is off → this closes the normally closed key


What Do We Have?

- A Buzzer

- A Clock

 

- An Oscillator

 

(symbol)

Oscillator




- **Period** of oscillator
- Frequency: cycles per second
- Unit: 1 cycle per second: 1 Hertz
- Modern computes:
Billions of Hertz = Gigahertz (GHz)




Heinrich Hertz
1857--1894

flip flop


Another Contraption

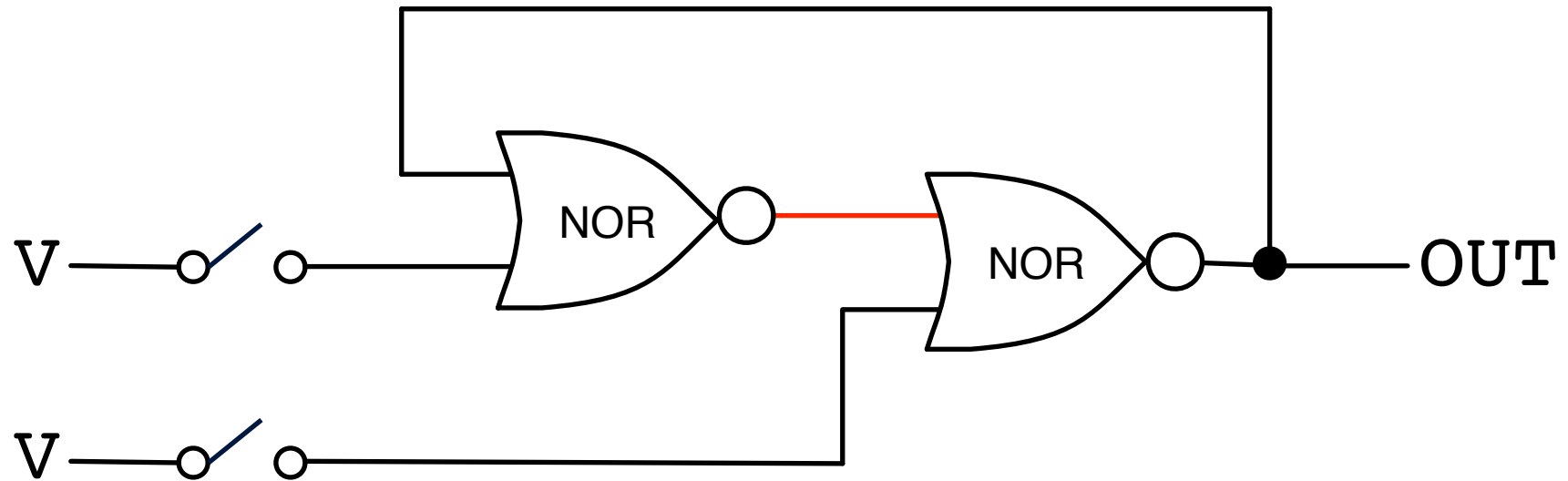

Closing Upper Key

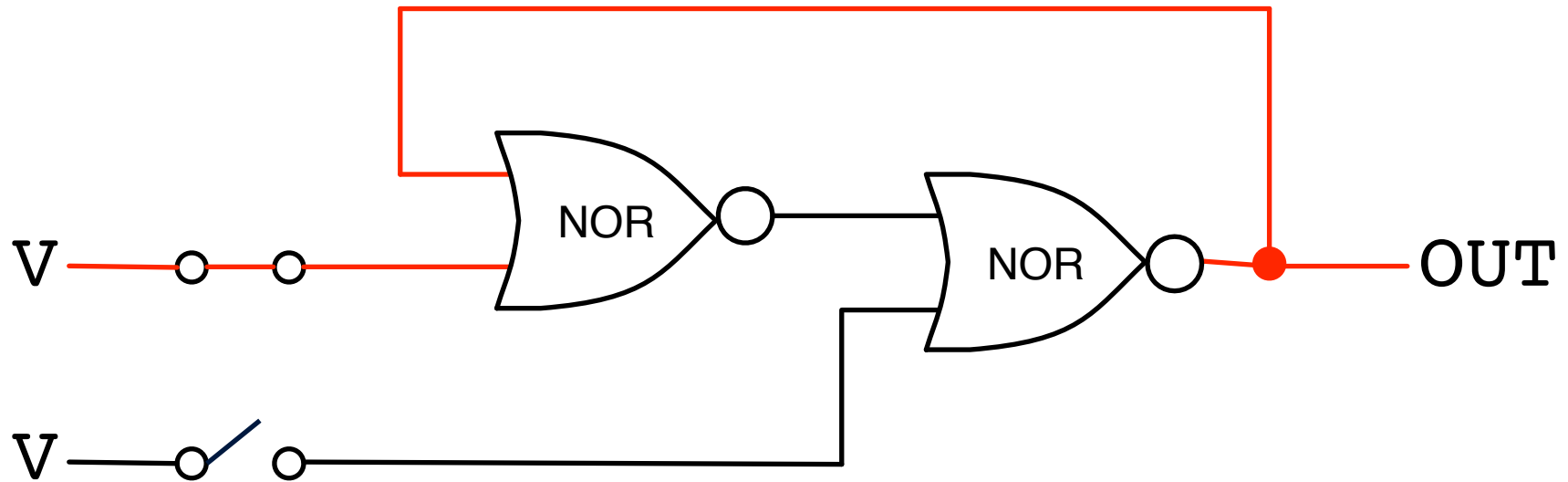


Opening Upper Key

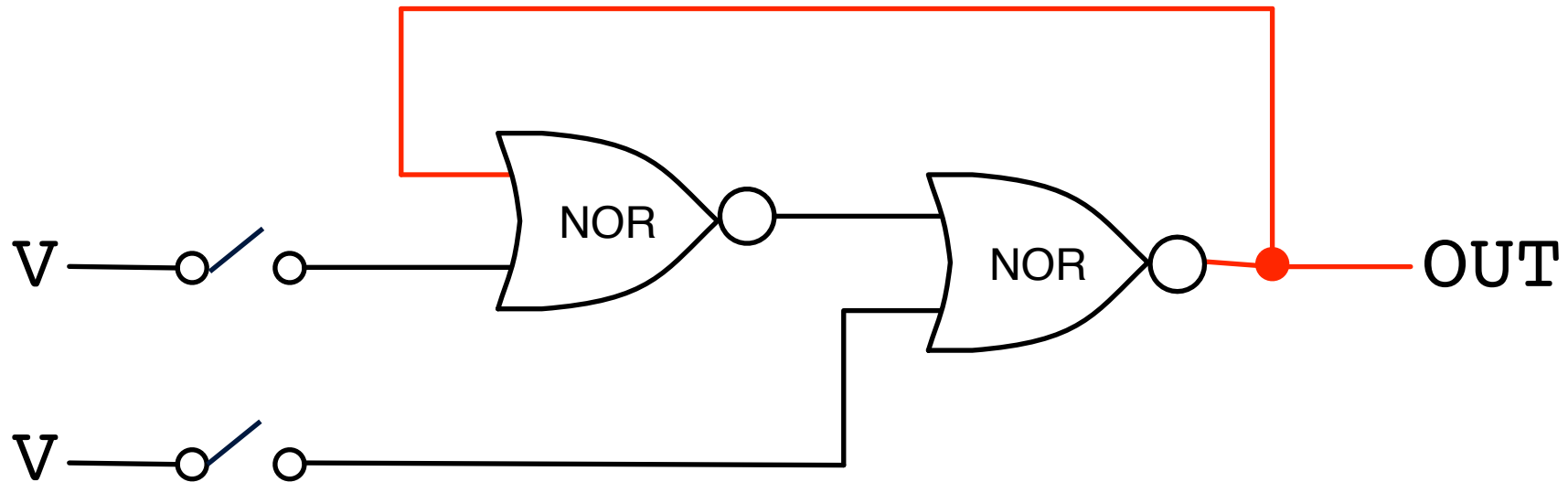


Same key configuration as initially

But: Now OUT is on --- we **remembered** the key turn

Closing Lower Key

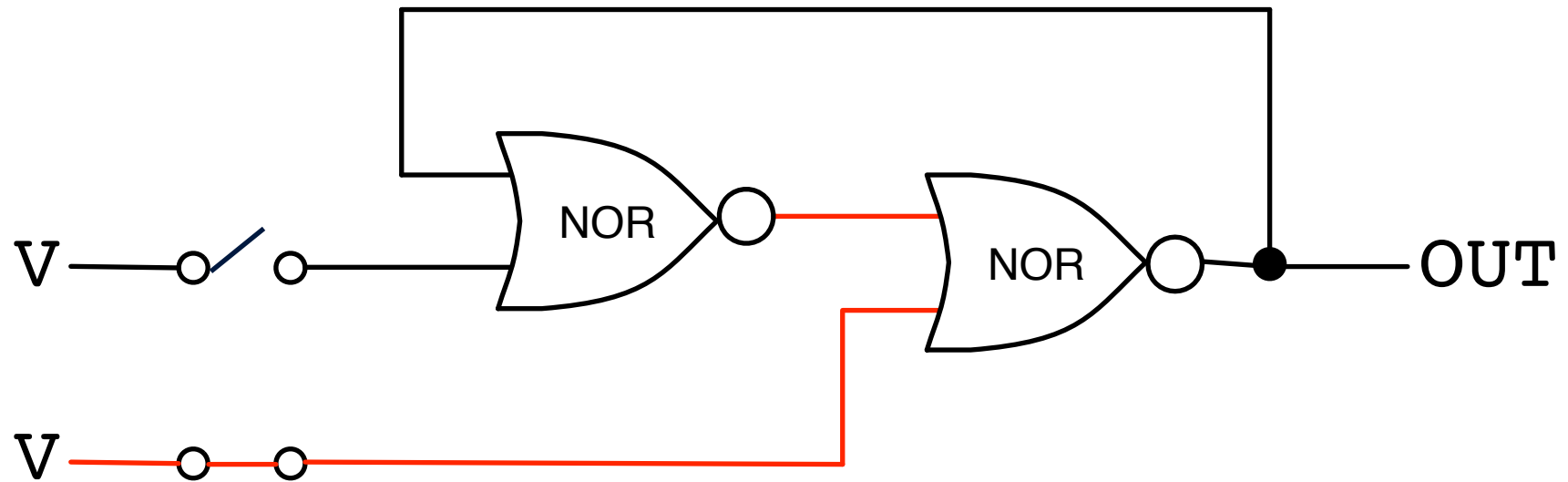

Opening Lower Key

 

Back to initial state


Memory

- We have memory -- called **Reset-Set Flip-Flop**
- Truth table


UPPER	LOWER	OUT
0	0	OUT
0	1	0
1	0	1
1	1	Illegal

- UPPER = SET
- LOWER = RESET

Re-Arranged

 

Symmetric

 

Truth Table


S	R	Q	\bar{Q}
1	0	1	0
0	1	0	1
0	0	Q	\bar{Q}
1	1	Illegal	




d-type flip flop

- Control bit ("clock")
 - on = write to memory
 - off = read from memory
- Data bit
 - data item to be written
- Output
 - current state of the memory

Replace Set/Reset with Data

 

Add Control Bit ("Clock")

 

D-Type Flip-Flop

- Also called **D-type latch**
- Circuit latches on one bit of memory and keeps it around
- Truth table

Data	Clock	Q	\bar{Q}
0	1	0	1
1	1	1	0
X	0	Q	\bar{Q}

- Can also build these for multiple data bits



accumulative adder

Design Goal




- Adder has initially value 0
- Adding a number
→ value increases
- Resetting
→ value goes back to 0

Ingredients




Ingredients

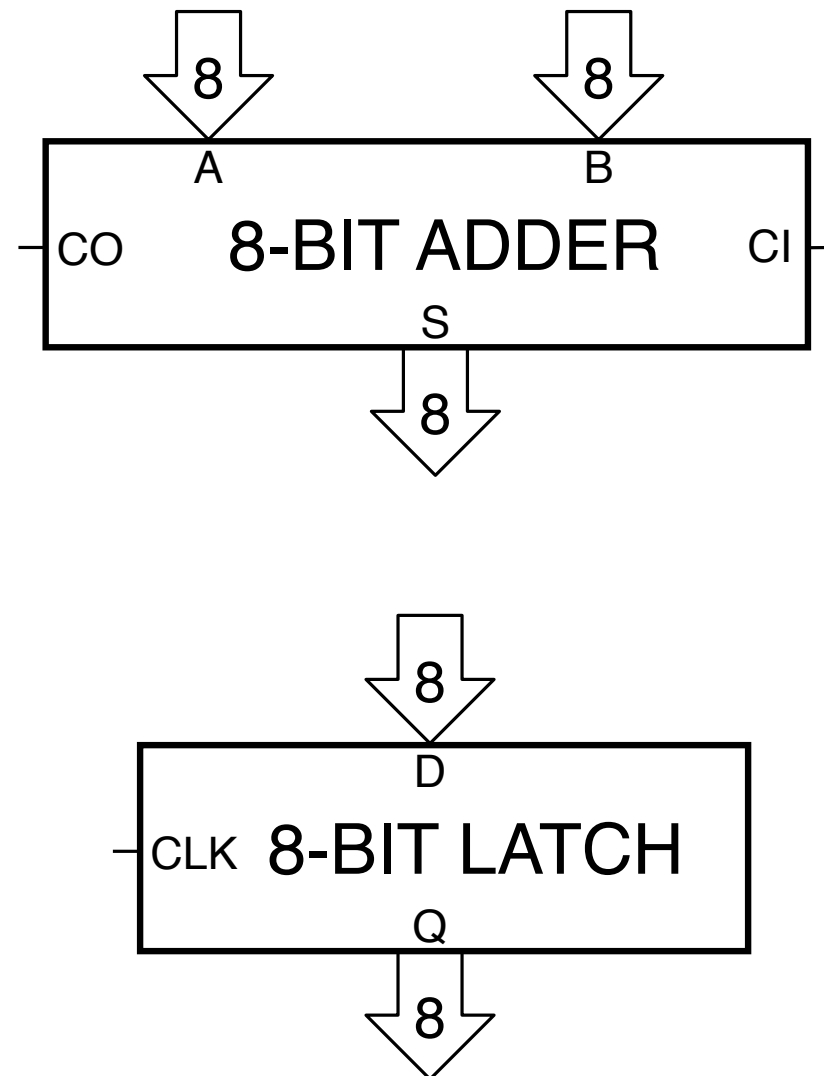


Building an Accumulative Adder

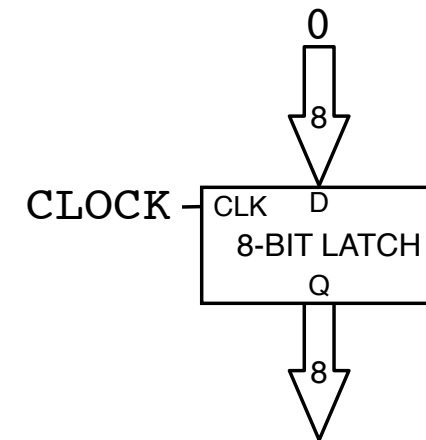- Latch: current sum
- Clock on \rightarrow set it to 0




Building an Accumulative Adder

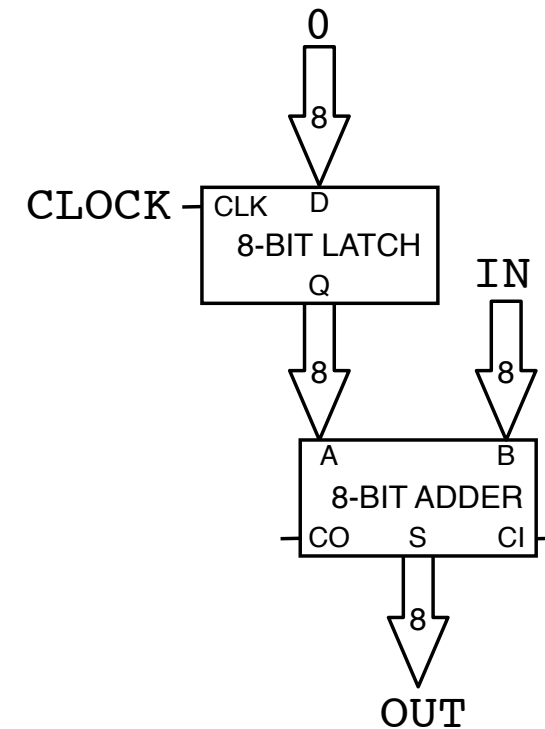- Adder
- Combines
 - current value
 - selected input



Building an Accumulative Adder

 
- Can we pass output directly to latch?
- Concerns
 - select between 0 and sum
 - only stored when clock on



Building an Accumulative Adder


- 2-1 selector
- Either uses 0 or sum
- Built with AND gates

- Still have runaway feedback loop...

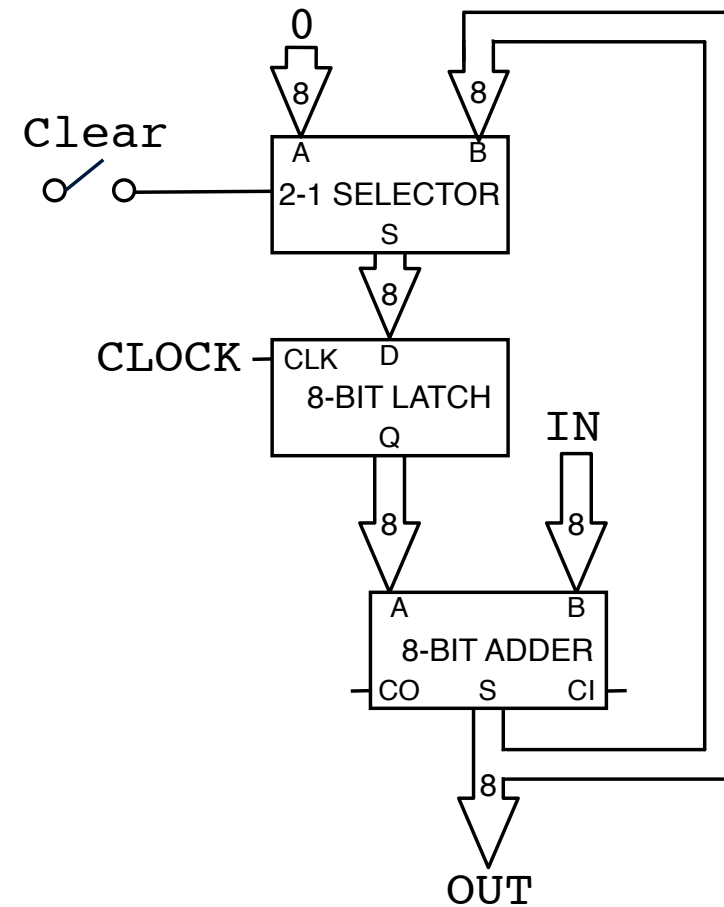


Building an Accumulative Adder

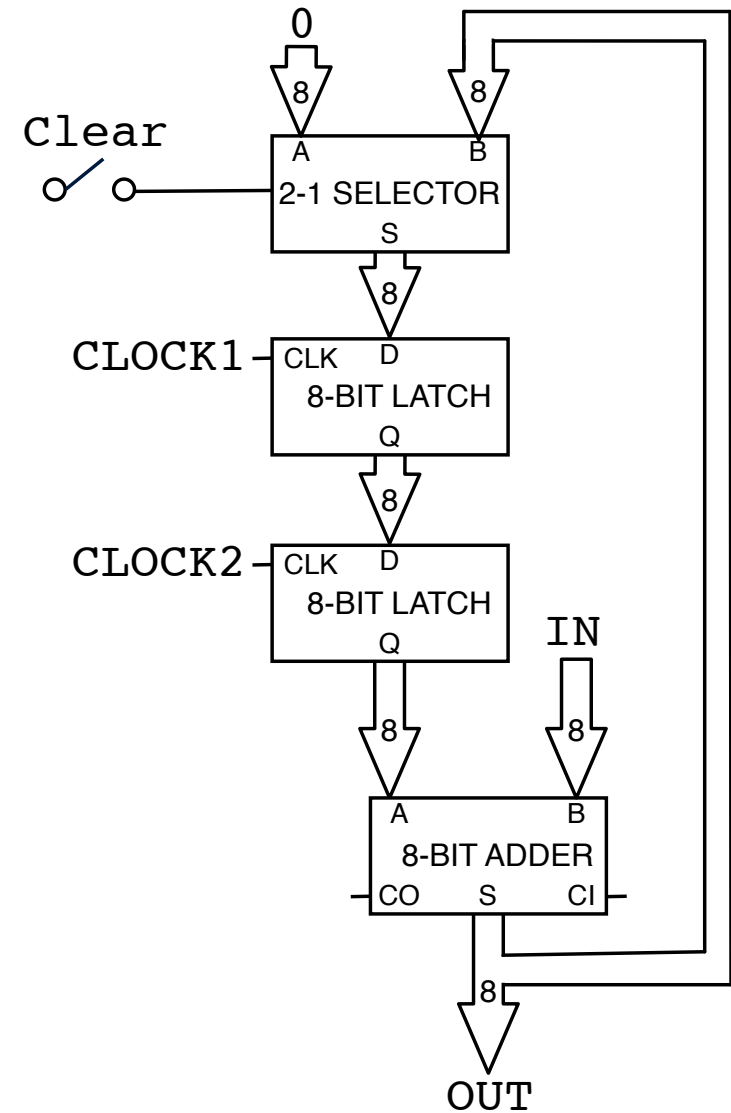- Two Latches
 - one to store the sum
 - one to store input to adder
- Clock 1
 - carry out addition
 - store result
- Clock 2
 - transfer to set up next addition






Building an Accumulative Adder

 - Combine the clocks
- Pressing the add key
 - carry out addition
 - store result in upper latch
- Release the add key
 - transfer to lower latch
 - set up next addition




What Else?

- Remember the oscillator?

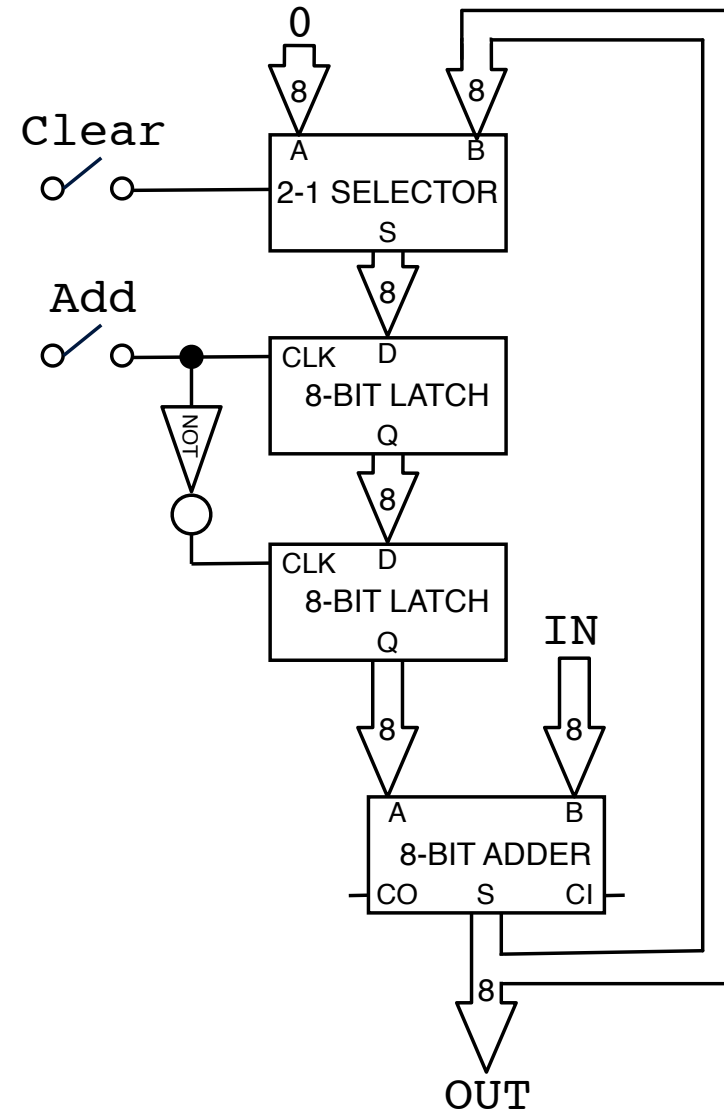  


What Else?

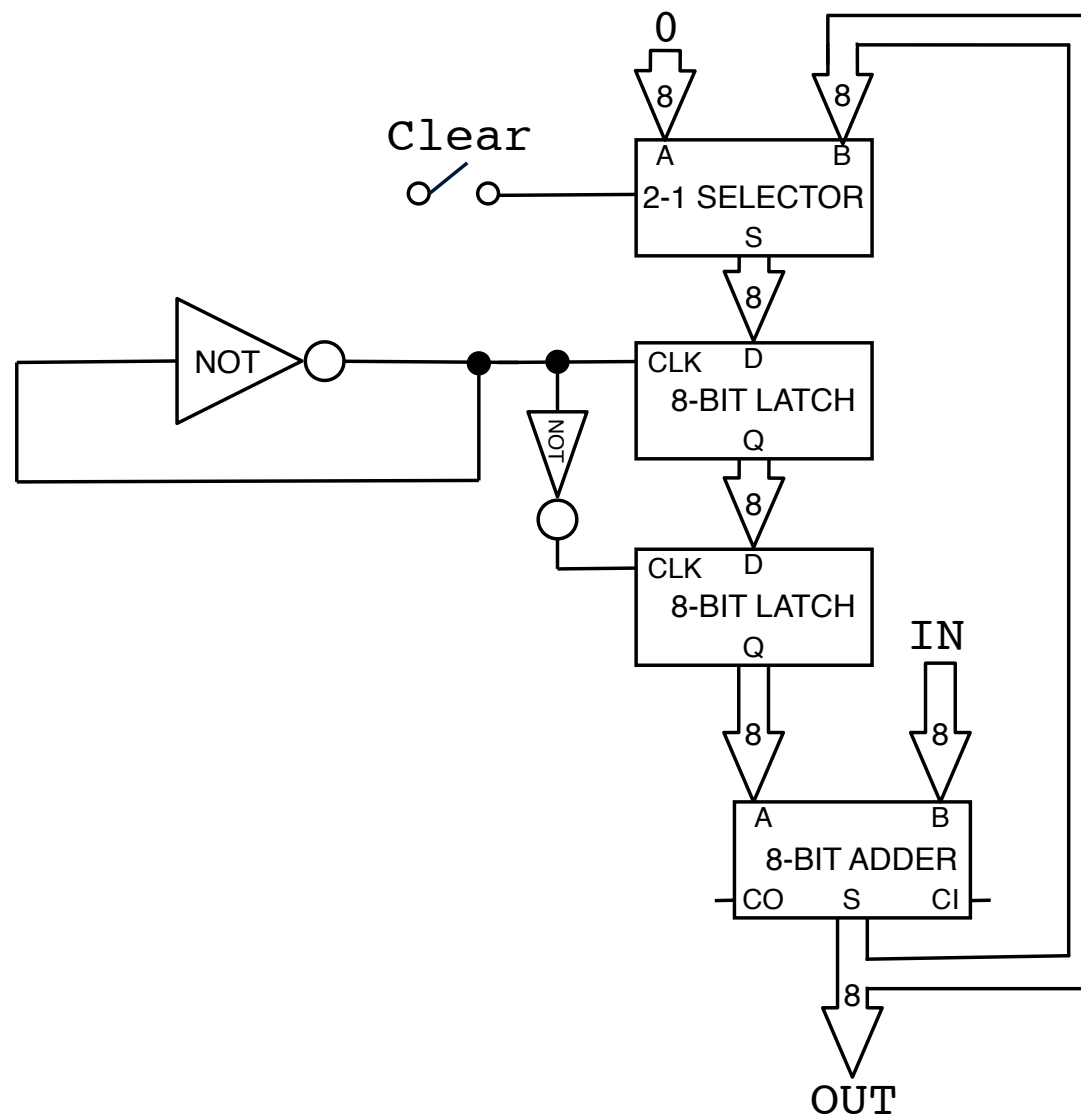

- Each cycle of oscillator:
keeps adding

What Else?

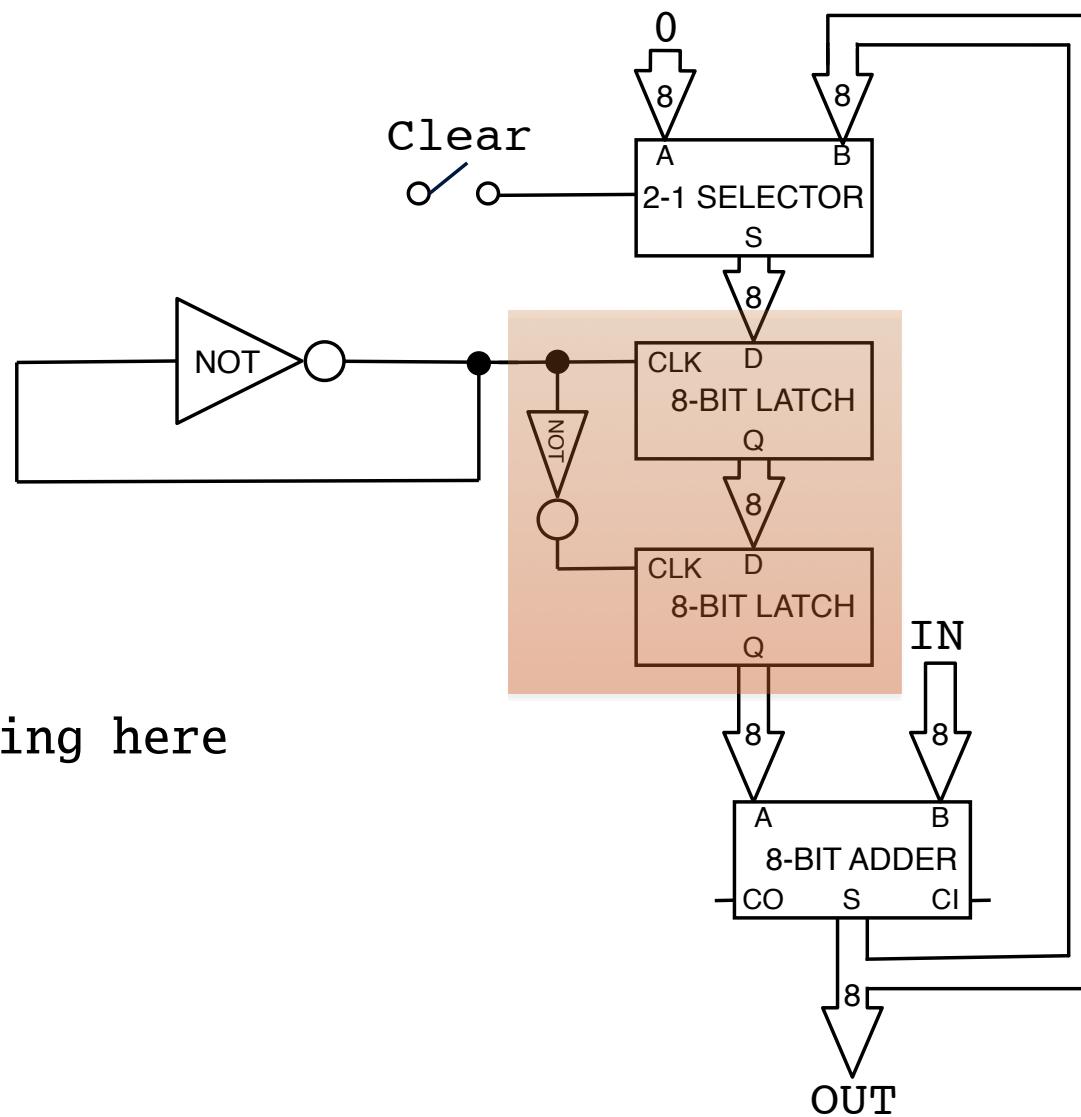

- We have something interesting here


edge triggered flip-flop

D-Type Latch



- When clock is on, save data
- "Level-triggered"

D-Type Latch

 

- "Edge-triggered": changes value, when *switched from 0 to 1*

Edge Triggered D-Type Latch



Symbol


Truth Table

Data	Clock	Q	\bar{Q}
0	↑	0	1
1	↑	1	0
X	0	Q	\bar{Q}




ripple counter

Oscillator and Latch

 

Data	Clock	Q	\bar{Q}
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1


Oscillator and Latch

 



Data	Clock	Q	\bar{Q}
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1

Halving of Frequency

Data	Clock	Q	\bar{Q}
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1

 

Multiple Bits

 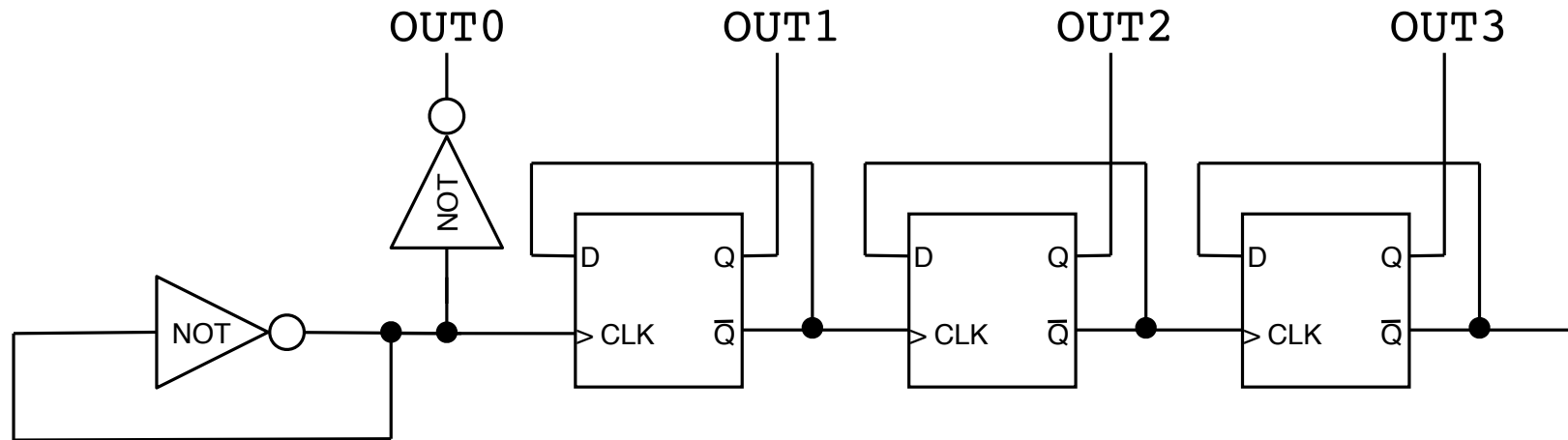

Ripple Counter

